

NOTES

The basic connections of the transistor in amplifier circuits.

The common base configuration .

The common base configuration is shown in Fig (68) . The input and output of the circuit have a common Base . The current relationships (from section) can be written as follows :

$$I_c = \alpha I_E + I_{CBO} \quad ;$$


I_{CBO} being the leakage current , due to the fact that the emitter/base junction is open circuited ---> reverse biased , and ,

$$I_B = (1-\alpha) I_E$$

and ,

$$I_c = \alpha I_E$$


Fig(68)

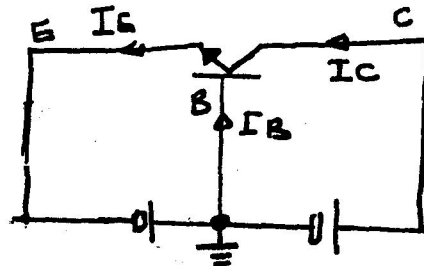


5.4.1.1 The common base static characteristic curves :

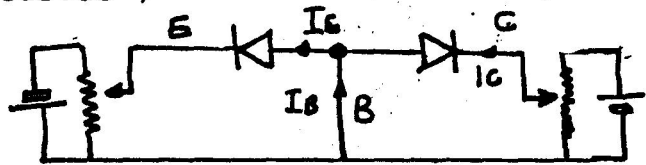(a) The input characteristic curves ;

referring to Fig (69) , The input characteristic curves are found by determining the relationship (curves) between I_E and V_{BE} (input circuit) , for a given set of values of V_{CB} . Such curves are shown in Fig (70) . With V_{CB} open circuited , the base/emitter junction behaves as forward biased . As V_{CB} is increased , the depletion layer of the base/collector junction increases , causing a reduction of the effective base layer width (The early effect ---- see reference book for more details) , causing an increase in the value of



Fig(69)

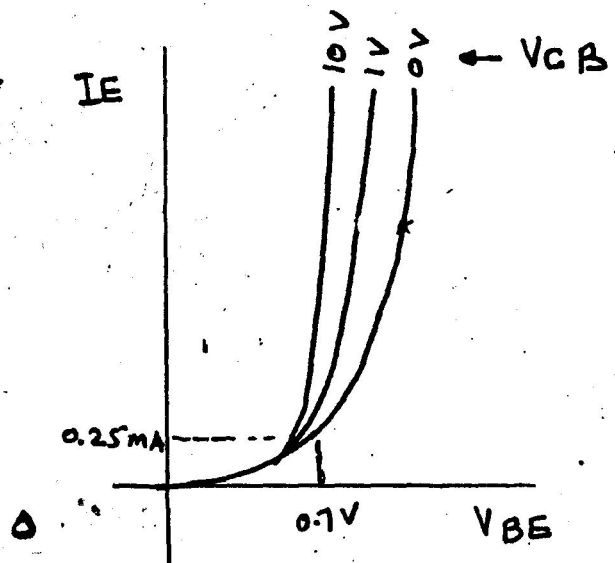

Fig(70)

IE and intern , an increase in the IE for a given VBE . It should be pointed at this stage , that the gradient of the an input characteristic curve , at a given operating point defined by I_{E0} and V_{CB0} , has a dimension of resistance , i.e.

$$\Delta V_{EB} / \Delta I_E \quad | \quad \text{at } Q \text{ point}$$

This is known as the input resistance h_{ib} (b denotes the common base configuration) .


(B) The output characteristics

In obtaining these curves , relationships between I_c and V_{CB} for given values of I_E are obtained as shown in Fig (71) .

Such curves depicts three distinct regions :

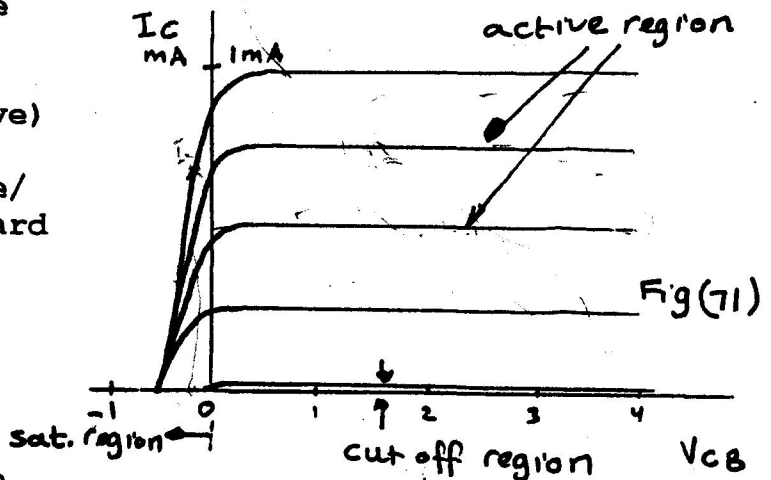(1) The operating (Active) region.


In this region , the base/emitter junction is forward biased , while the base/collector junction is reversed biased , i.e.



$I_c = I_E$ (approximately

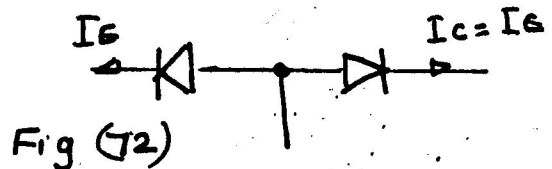(2) The saturation region

As a negative V_{CB} is applied , the collector/base junction become forward biased, injection current as shown , fig (72), i.e. the resultant I_c drops to zero .



(3) the cutoff region

In this region , both transistor junctions are reversed biased , i.e. no current flow , except for the leakage current I_{CBO} .

As in the case of the input circuit , the gradient at a particular operating point (I_c , V_{CB}) is given by ;

$$\Delta I_c / \Delta V_{BC} \quad | \quad \text{at } Q \text{ point}$$

This is known as the output conductance of the transistor and is denoted by h_{ob} (b denotes the common base connection) , i.e. , the output resistance = $1 / h_{ob}$

i.e. the CB Transistor configuration has low input resistance (impedance) and a high output resistance , which makes coupling between stages difficult .

4.3,
5.4.2 The common emitter configuration

In this configuration , shown in Fig (73) , , the base of the transistor is arranged as the input terminal and the collector as the output terminal , with the emitter being common to both input and output of the circuit .

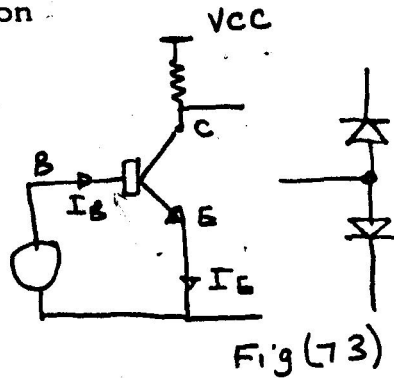


Fig (73)

Using similar procedures to that outlined in the common base configuration , we have ,

$$I_B = (1 - \alpha) / \alpha * I_C$$

or ,

$$I_B = I_C / \beta = I_C / H_{FE}$$

and since $I_E = I_C + I_B$ then , from simple manipulation of the above equation and adding the component of the leakage current derived for the common base configuration (from $I_C = \alpha I_E + I_{CBO}$), would yield ;

$$I_C = \alpha (I_C + I_B) + I_{CBO} \quad \therefore I_C [1 - \alpha] = \alpha I_B + I_{CBO}$$

$$I_C = \alpha I_B / (1 - \alpha) + I_{CBO} / (1 - \alpha)$$


the term $I_{CBO} / (1 - \alpha)$ is called the leakage current in the common emitter mode with I_B set equal to zero) and is denoted by I_{CEO}

It is clear that $I_{CEO} / (1 - \alpha)$ approximately equals $\beta * I_{CBO}$, for $\alpha \approx 1$.
i.e. the leakage current in the common emitter case is much larger than the common base case , by a factor of β

5.4.2.1 The common emitter static characteristics at $V_{CE} = 10V$ & V_{CE}

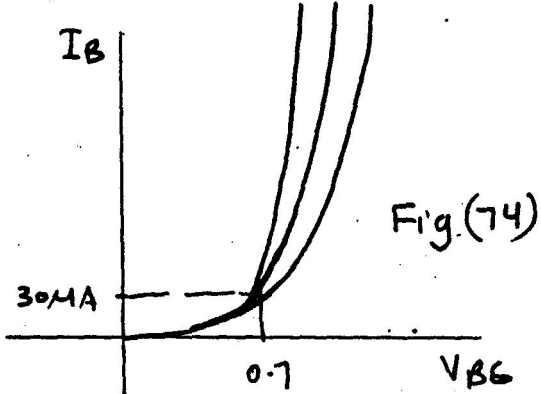(a) The input characteristics ;


considering the following curves, Fig (74) , (V_{BE} against I_B), then we observe that for $V_{CE} = 0$ and $V_{BE} = 0$ then $I_B = 0$, since both diodes are reversed biased . If V_{CE} is kept at zero level and



V_{BE} is increased then rapid increase in the I_B occurs and the combined diode behaves as a simple forward biased diode, as shown in Fig (75). As V_{CE} is further increased (with V_{BE} remains constant) the value of I_B decreases (because one diode, BC, is reversed biased and the other diode, BE, is forward biased).

The static input resistance of the transistor in this configuration = V_{BE} / I_B at any point on the curve. This value would vary very widely, depending on which part of the curve the quantity is evaluated. On the other hand, the small signal dynamic (operating) resistance is important and is given by:

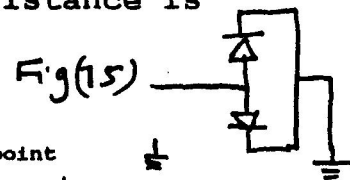
$$\Delta V_{BE} / \Delta I_B \text{ at } Q \text{ point} = h_{ie} = V_T / I_B \text{ at } Q \text{ point} = 26 \text{ mV} / I_B \text{ at room temperature}$$



temperature, see reference book on how these equations were derived.

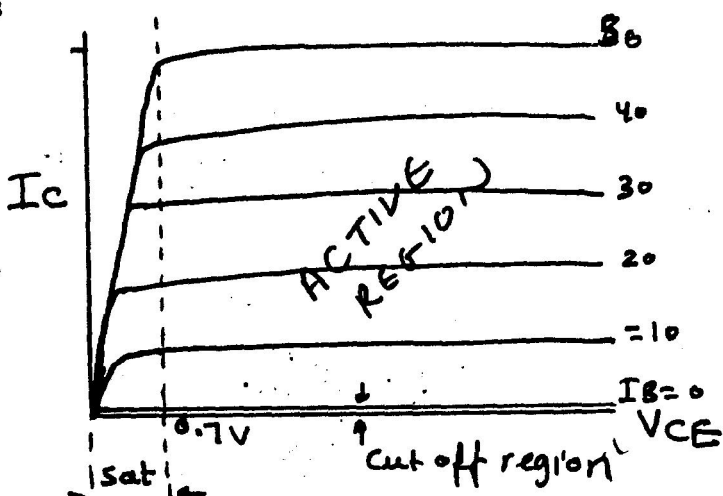(b) The output characteristics

The following set of curves, Fig (76), illustrate the way in which the collector current I_C varies with the collector voltage, for a given values of base currents. Such curves are called the output characteristic curves of the transistor in the common emitter configuration. The curves display three distinct regions:



(1) The Active region.

In this region, the collector/emitter voltage exert little control on the collector current, due to the fact that, the collector/base junction is reversed biased and thus does not contribute to the I_C and I_E current which result from the forward bias of the base/emitter junction.


If the transistor is to be used as a linear amplifier, it must be used in this region (the equations relating the currents of the transistor and which were presented at the beginning of this section, are applicable in this region).

IN this region, three parameters are of interest; [1.1] The gradient of a particular curve, for a given I_B and V_{CE} is given by:

$$\Delta I_C / \Delta V_{CE} = h_{oe} = \text{the output conductance of the}$$

transistor in the common emitter configuration, thus the output resistance = $1 / h_{oe}$ (the e denotes the common emitter connection)

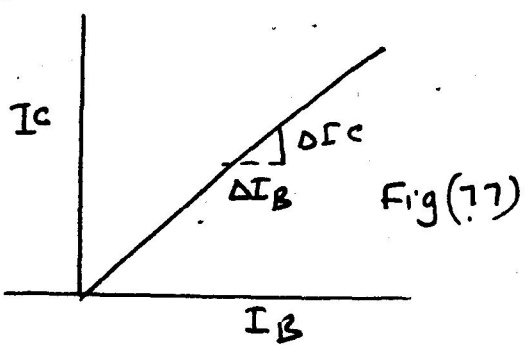[1.2] If we construct a plot of I_c against I_b , Fig (77), using the output characteristic curves, then the gradient of the resulting curve would yield a quantity given by :




$\Delta I_c / \Delta I_b | V_{ce} = \text{constant}$
 $= h_{fe}$
 $=$ the dynamic operating current gain of the transistor (not to be confused with the static current gain H_{FE}).

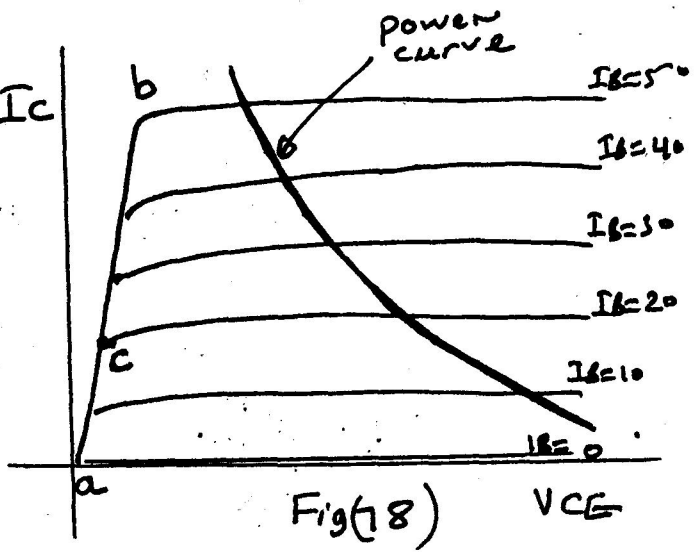[1.3] The safe power operating range

In using the transistor, the maximum power dissipated (as specified by the manufacturers) should not be exceeded.


A maximum power curve, Fig (78), for variable V_{ce} and I_c , can be constructed on the same set of output characteristic curves (hyperbola $V_{ce} \cdot I_c = \text{constant}$). In order that the power is not exceeded, the transistor must be operated to the left of the power curve.



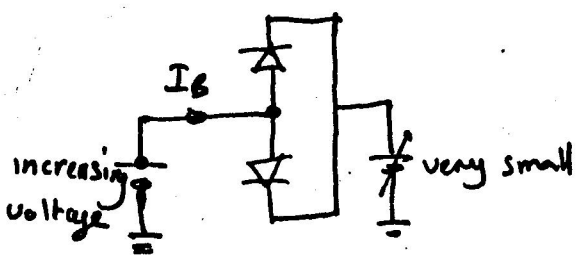(2) The saturation region .

Point C on the curve Fig (76), corresponds to a base current equals or greater than 20 mA . It follows that the collector current does not increase in value with any increase in


base current . Such analogy applies to the A B portion of the curves and is identified as the saturation region of the common emitter configuration . In this region both the base/emitter and base/collector diodes are forward biased as shown in Fig (79)..



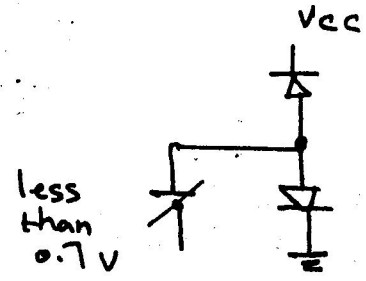(3) The cut off region .




When the base current is zero, virually no collector current willflow. This part of the output characteristic curves is called the cut off region and both diodes (junctions) of the transistor are reversed biased as shown in Fig (80).



Fig(80)

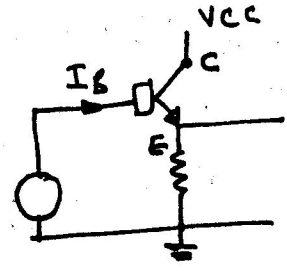4. y
5.4.3 The common collector configuration (Emitter follower)

Referring to Fig (81) which shows a typical common collector circuit. Such circuit is essentially the same as the common emitter circuit, except that the load resistor is in the emitter lead rather than in the collector lead. If we continue to specify the operation of the circuit in terms of currents which flow in it, then the operation will be tha same as that of the common emitter configuration. When no base current flows in the circuit (except for leakage) then the emitter current will also be zero and thus no current will flow in the load. As I_b is increased from zero value, the transistor will pass through the active stage and eventually reach saturation. In this case, most of VCC will appear across the load resistor (- 0.2 V).



Fig(81)