

An Najah University – Faculty of engineering  
 Electrical Eng. Department  
 System and Signals

Instructor: Jamal Khrousheh

10.5  
 1st hr. Exam  
 summer 2009

Question #1 (10 mark)


Periodic signal has the following Fourier series

$$f(t) = \sum_{n=1}^3 \frac{1}{n+1} \cos(nw_0 t) + \sum_{n=1}^3 \frac{2}{n} \sin(nw_0 t)$$

$$I(t) = \sum_{n=1}^3 (n \cos(nw_0 t + \theta_n))$$

Where  $w_0 = 2$  rad/sec

O-7Q6

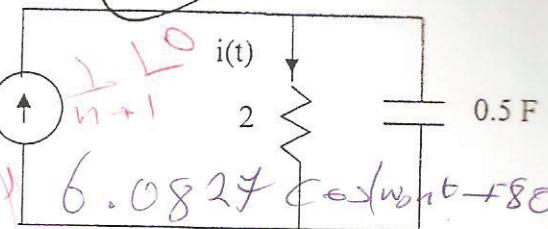

Find: 1- sketch spectrum "magnitude and Phase" for  $C_n$  "complex coefficients" for the periodic signal

2- The signal applied to the circuit shown, find  $i(t)$


3- What is the power dissipated on the resistance

$$w_0 = \frac{2\pi}{T} \Rightarrow T = \frac{2\pi}{w_0}, \quad T = \pi$$

$$C_n = \frac{1}{\pi} \int_0^\pi i(t) e^{-jn\omega_0 t} dt = \frac{1}{\pi} \int_0^\pi \left( \sum_{n=1}^3 \frac{1}{n+1} \cos(n2t) + \sum_{n=1}^3 \frac{2}{n} \sin(n2t) \right) e^{-jn\omega_0 t} dt$$

$$\text{let } u = \cos n2t \quad du = -j2n \sin n2t dt$$
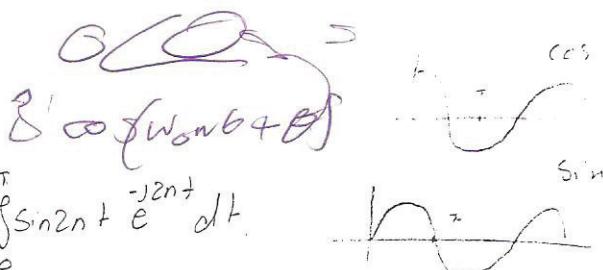
$$du = -\frac{j}{2n} \sin n2t dt \quad v = \frac{1}{-j2n} e^{-jn\omega_0 t}$$



$$\text{let } u = \sin n2t \quad du = j2n \cos n2t dt$$

$$du = \frac{j}{2n} \cos n2t dt \quad v = \frac{j}{2n} e^{-jn\omega_0 t}$$

$$\Rightarrow \int_0^\pi \cos n2t e^{-jn\omega_0 t} dt = \int_0^\pi \cos n2t \left[ \frac{j}{2n} e^{-jn\omega_0 t} \right] + \frac{j}{4n^2} \int_0^\pi \sin n2t e^{-jn\omega_0 t} dt$$

$$\frac{16n^4 + j^2}{16n^4} \int_0^\pi \cos n2t e^{-jn\omega_0 t} dt = \left[ \frac{j}{2n} e^{-jn\omega_0 t} - \frac{1}{2n} \right] \Rightarrow \int_0^\pi \cos n2t e^{-jn\omega_0 t} dt = \frac{j(e^{-jn\pi} - 1)}{2n} + \frac{16n^4}{16n^4 + j^2}$$

$$\int_0^\pi \sin n2t e^{-jn\omega_0 t} dt = \text{let } u = \sin n2t \quad du = j2n \cos n2t dt$$

$$= \int_0^\pi \cos n2t \left[ \frac{j}{2n} e^{-jn\omega_0 t} \right] dt = \frac{j}{2n} \int_0^\pi \cos n2t e^{-jn\omega_0 t} dt$$

$$= \frac{-j^2}{8n^3} \cos n2t \left[ e^{-jn\omega_0 t} \right] \Big|_0^\pi - \frac{j^2}{16n^4} \int_0^\pi \sin n2t e^{-jn\omega_0 t} dt$$

$$\frac{16n^4 + j^2}{2n \cdot 16n^4 + j^2} \int_0^\pi \sin n2t e^{-jn\omega_0 t} dt = \frac{-j^2}{8n^3} e^{-jn\pi} - \frac{j^2}{8n^3} = -\frac{j^2(e^{-jn\pi} - 1)}{8n^3}$$

$$\int_0^\pi \sin n2t e^{-jn\omega_0 t} dt = \frac{2n}{16n^4 + j^2} \cdot -j^2 \left( e^{-jn\pi} + 1 \right) = \frac{2n}{16n^4 + j^2} \left( e^{-jn\pi} + 1 \right)$$

$$C_n = \frac{1}{\pi(n+1)} \cdot \frac{j8n^3}{16n^4 + j^2} \left( e^{-jn\pi} - 1 \right) + \cancel{\frac{4n}{16n^4 + j^2} \left( e^{-jn\pi} + 1 \right)} =$$

$$\frac{1}{\pi(16n^4 + j^2)} \left[ \frac{j8n^3}{n+1} \left( e^{-jn\pi} - 1 \right) + 4e^{-jn\pi} + 4 \right]$$


Question # 2 (10 mark)

For the circuit shown:

If  $V_{in}(t) = \delta(t-1)$  applied to the input, what is  $V_c(t)$

$$j_{72} = V_{in}(j\omega) = \frac{e^{-(t-1)}}{2 + \frac{1}{j\omega}} \mu(t-1)$$
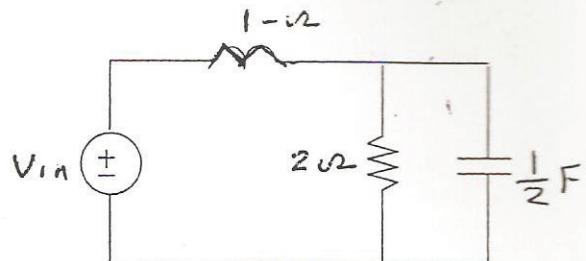
$$V_c(t) = \frac{2}{3} e^{-(t-1)} \mu(t-1)$$




b) for system shown, find and sketch  $i(t)$ , knowing that  $V_{in}(t)$  given by the following signal

$$1 - z(j\omega) = \frac{1}{j\omega}$$

$$2 - z(j\omega) = e^{j2\omega}$$


$$V_{in}(j\omega) = \int_{-\infty}^{\omega} f(t) e^{-j\omega t} dt = \int_1^{\omega} e^{-j\omega t} dt = \left[ \frac{1}{-j\omega} e^{-j\omega t} \right]_1^{\omega}$$
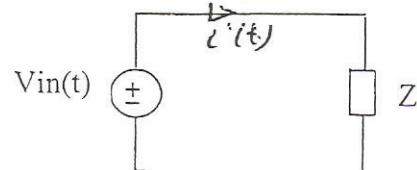
$$V_{in}(j\omega) = \frac{1}{-j\omega} [e^{-j\omega\omega} - e^{-j\omega}]$$



$$I(j\omega) = \frac{V_{in}(j\omega)}{z(j\omega)} = \frac{1}{-j4\omega} [e^{-j\omega} - e^{-j2\omega}] = \frac{-j\omega}{e^{-j\omega} - e^{-j2\omega}}$$




$$I(t) = \delta(t-1) - \delta(t-2)$$

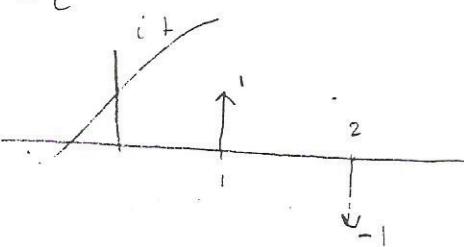

$$I(j\omega) = \frac{1}{-j\omega} [e^{-j\omega} - e^{-j2\omega}] * e^{-j2\omega} = \frac{-j4\omega}{-j\omega+0} + \frac{j3\omega}{j\omega+0}$$

$$I(t) = -\frac{1}{2} \text{sgn}(t-4) + \frac{1}{2} \text{sgn}(t-3)$$

$\text{sgn}(t-4)$

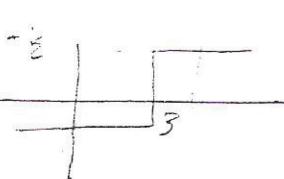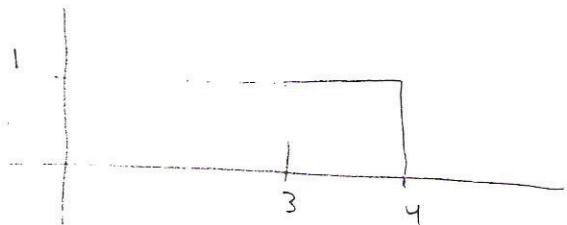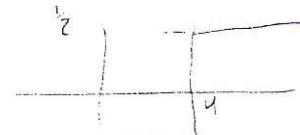


$\text{sgn}(t-3)$

$$3(\text{sgn}(t-4) - \text{sgn}(t-3)) = 1$$

Question # (5 marks)

For system shown knowing that  $V_{in}(t)$  is the input and  $V_o(t)$  is the output:


Find  $h(t)$

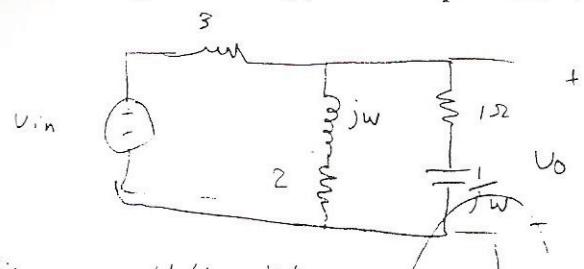


$$V_o = \frac{2 + j\omega}{5 + j\omega} \cdot V_{in} \Rightarrow \frac{V_o(j\omega)}{V_{in}(j\omega)} H(j\omega) = \frac{2 + j\omega}{5 + j\omega}$$

$$H(j\omega) = 1 - \frac{3}{5 + j\omega}$$
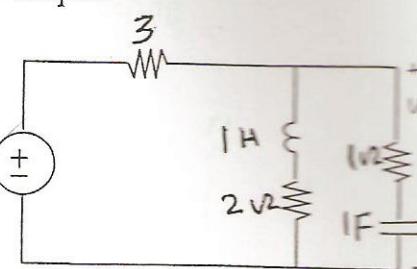
$$h(t) = [8/7] - 3 e^{-5t} \rightarrow u(t)$$


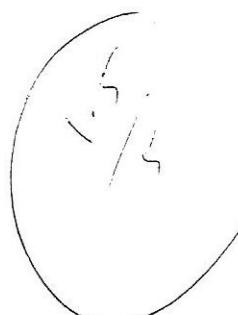
$$\frac{5 + j\omega}{5 + j\omega} \frac{1}{2 + j\omega} = \frac{5 + j\omega}{7 + j\omega} - \frac{3}{7 + j\omega}$$



$V_o$